




MODERN SCIENCE ACADEMY

16. "BASIC ELECTRONICS"

Choose the correct answers from the following choices.

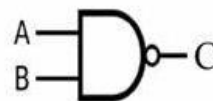- 1) The process by which electrons are emitted by a hot metal surface is known as:
(a) boiling (b) evaporation (c) conduction (d) thermionic emission
- 2) The particles emitted from a hot cathode surface are:
(a) positive ions (b) negative ions (c) protons (d) electrons
- 3) The logical operation performed by this gate is:
(a) AND (b) NOR (c) NAND (d) OR
- 4) AND Gate can be formed by using two:
(a) NOT gates (b) OR gates (c) NOR gates (d) NAND gates
- 5) The output of a two input NOR gate is 1 when:
(a) A=1 and B=0 (b) A=0 and B=1 (c) both A and B are 0 (d) both A and B are 1
- 6) If $X=A.B$, the X is 1 when:
(a) A and B are 1 (b) A or B is 0 (c) A=0 and B=1 (d) A=1 and B=0
- 7) The output of a NAND gate is 0 when:
(a) both of its inputs are zero (c) any of its inputs is 0
(b) both of its inputs are 1 (d) any of its inputs is 1
- 8) The biggest achievement of electronics is:
(a) calculator (b) transistor (c) computer (d) mobile
- 9) Typical value of the voltage and current used for thermionic emission from tungsten filament is:
(a) 6V and 0.3A (b) 12V and 0.3A (c) 12V and 3A (d) 6V and 3A
- 10) The screen of CRO is made up of:
(a) Zinc (b) Iron (c) Phosphor (d) Glass
- 11) The brightness of spot on CRO fluorescent screen is controlled by:
(a) anode (b) grid (c) plates (d) cathode
- 12) In CRO, the potential of grid is:
(a) Zero (b) positive (c) negative (d) neutral
- 13) George Boole invented:
(a) Geometry (b) Calculus (c) Trigonometry (d) Boolean Algebra
- 14) Boolean expression for AND operation is:
(a) $X=A+B$ (b) $X=\overline{A+B}$ (c) $X=A.B$ (d) $X=A+B$
- 15) Which logic gate is similar to two series switches?
(a) AND (b) OR (c) NAND (d) NOR
- 16) NOT gate is also called:
(a) convertor (b) invertor (c) adder (d) subtractor
- 17) Number of input terminals in NOT gate is:
(a) 1 (b) 2 (c) 3 (d) 4
- 18) Which gate is used to make burglar alarm?
(a) OR gate (b) AND gate (c) NAND Gate (d) NOR gate
- 19) Boolean expression for NOR gate:
(a) $X=A+B$ (b) $X=\overline{A+B}$ (c) $X=\overline{A.B}$ (d) $X=A.B$
- 20) If electric field is applied parallel to its direction of electron beam, the electrons will:
(a) speed up (b) slow down (c) deflect (d) none
- 21) If magnetic field is applied parallel to its direction of electron beam, the electrons will:
(a) speed up (b) slow down (c) deflect (d) none







MODERN SCIENCE ACADEMY

Important Short Questions

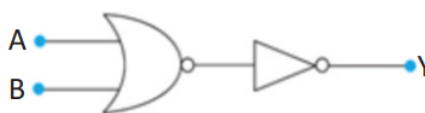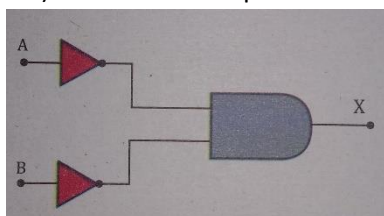- 1) What are free electrons?
- 2) What is meant by thermionic emission? Name two factors which can enhance thermionic emission?
- 3) Describe using diagrams, what happens when a narrow beam of electrons passes through a uniform electric field and a uniform magnetic field? What do these results indicate about charge on electron.
- 4) Give three reasons to support the evidence that cathode rays are negatively charged.
- 5) Why image is distorted when a magnet is brought close to the old television screens with CRT inside?
- 6) How can you control brightness of waveform on the screen of CRO?
- 7) What is the function of an accelerating anode in an electron gun?
- 8) Considering an oscilloscope explain:-
 - i. How the filament is heated?
 - ii. Why the filament is heated?
 - iii. Why the anode potential is kept positive w.r.t the cathode potential?
 - iv. Why the large potential is applied between anode and cathode?
 - v. Why the tube is evacuated?
- 9) Differentiate between analogue and digital **quantities** by examples and graphs.
- 10) Differentiate between analogue and digital **electronics**. Write names of five analogue and digital devices.
- 11) Define ADC and DAC.
- 12) Write down some benefits of using digital electronics over analogue electronics.
- 13) Define Boolean algebra, truth tables and logic gates.
- 14) What are three universal logic gates? Give their symbols and truth tables.
- 15) What is NAND Gate? Draw its symbol and truth table.
- 16) What is NOR Gate? Draw its symbol and truth table.
- 17) What is the difference to produce a LOW(0) output for an OR gate and AND gate?
- 18) What is the difference to produce a HIGH(1) output for an OR gate and NOR gate?
- 19) Draw a logic circuit for the logic equation $X=A+\bar{B}$.
- 20) What are the outputs of the following three circuits:



“Important Long Questions”

- A. Describe the construction and working of electron gun?
- B. What is Cathode Ray Oscilloscope (CRO)? Describe the working of its different parts and its uses.
- C. What is the difference between analogue and digital electronics? (At least seven)